

Single Phase Meter Lab




Purpose: To demonstrate the operation of a single phase watt-hour meter under different loading conditions.

Equipment used in the experiments:

1. Single Phase Two Wire Watt-Hour Meter – Form 1S
2. 52 Watt Light Bulbs
3. Digital Multi-Meter
4. Clamp Ammeter
5. Inductor
6. Capacitor

EXPERIMENT #1

(Using One 52 Watt Light Bulb)

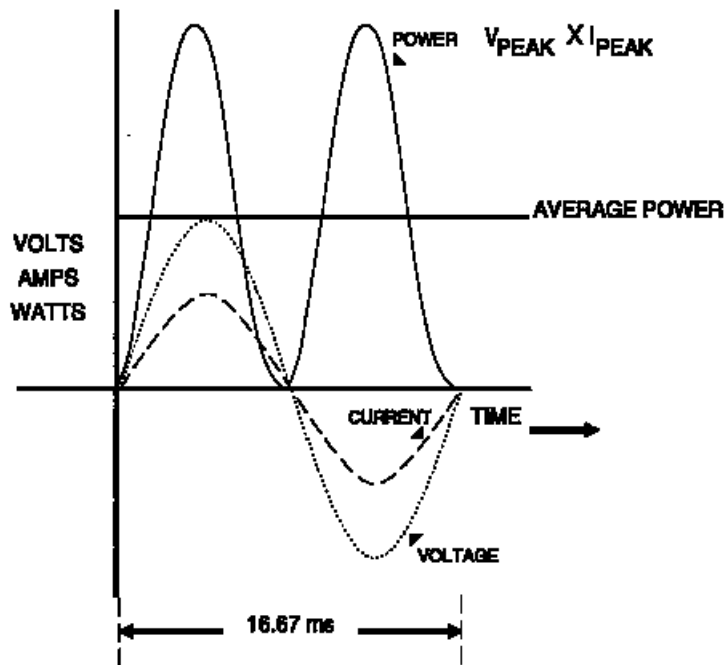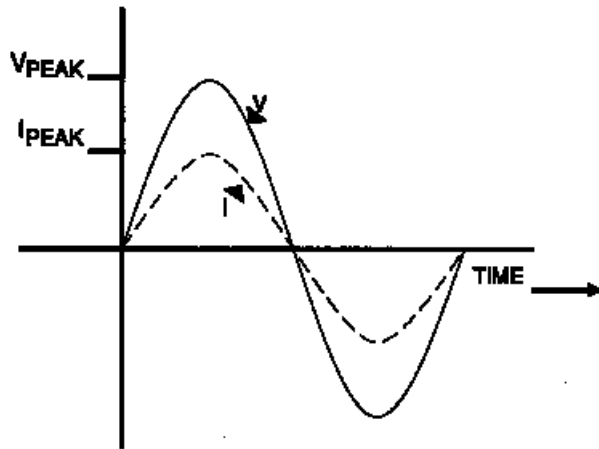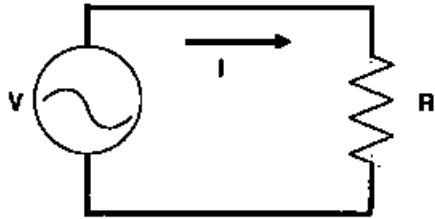

EXPERIMENT #1

(Using One 52 Watt Light Bulb)

1. Determine voltage across the load.
2. Determine current drawn by the load.
3. Calculate VA by Ohms Law.
4. Calculate power by watt load check.
5. Calculate load power factor and phase angle.

Formulas you may want to use.

$$VA = E \cdot I$$

$$P = E \cdot I \cdot \cos$$

$$WATTS = \frac{K_h \cdot Rev. \cdot 3600}{\text{time (sec.)}}$$

$$\frac{\text{Watts}}{VA} = \cos$$

$$\text{COS} \times 100 = \% \text{ Power Factor}$$

EXPERIMENT #2

(Using Two 52 Watt Light Bulbs)

1. Determine voltage across the load.
2. Determine current drawn by the load.
3. Calculate VA by Ohms Law.
5. Calculate power by watt load check.
5. Calculate load power factor and phase angle.

Formulas you may want to use.

$$VA = E \cdot I$$

$$P = E \cdot I \cdot \cos$$






$$WATTS = \frac{K_h \cdot Rev. \cdot 3600}{\text{time (sec.)}}$$

$$\frac{\text{Watts}}{VA} = \cos$$

$$\text{COS} \times 100 = \% \text{ Power Factor}$$

EXPERIMENT #3

(Using one Inductor)

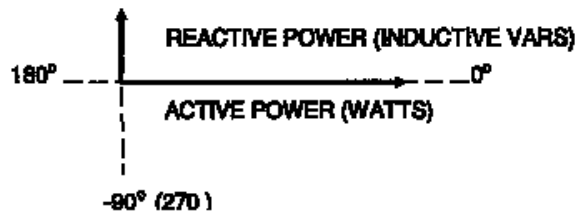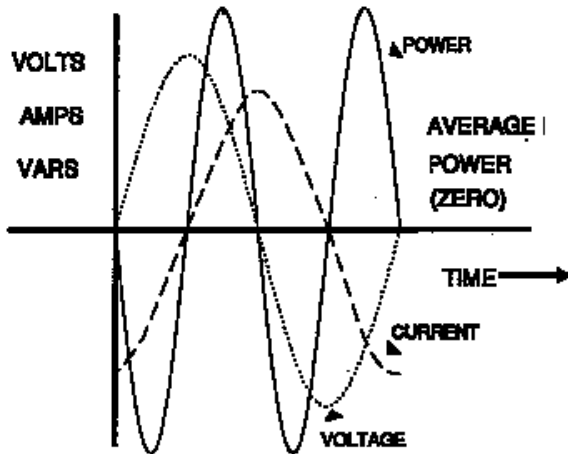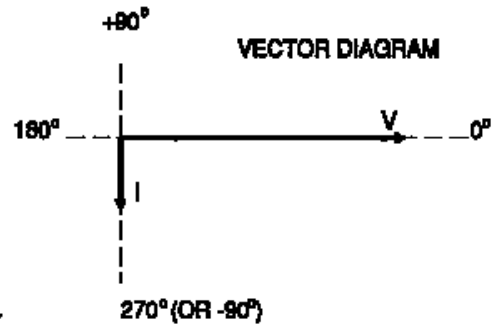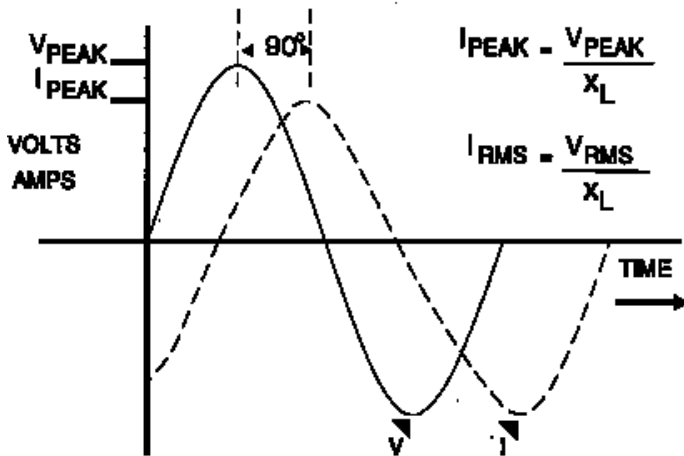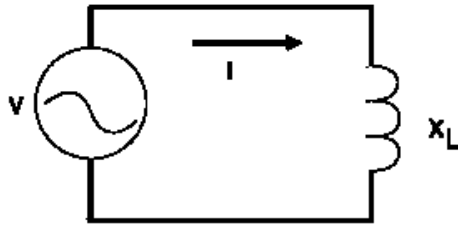

$+90^\circ$

EXPERIMENT #3

(Using the Inductor)

1. Determine voltage across the load.
2. Determine current drawn by the load.
3. Calculate VA by Ohms Law.
6. Calculate power by watt load check.
5. Calculate load power factor and phase angle.

Formulas you may want to use.

$$VA = E \cdot I$$

$$P = E \cdot I \cdot \cos$$







$$WATTS = \frac{K_h \cdot Rev. \cdot 3600}{\text{time (sec.)}}$$

$$\frac{\text{Watts}}{VA} = \cos$$

$$\text{COS} \times 100 = \% \text{ Power Factor}$$

EXPERIMENT #4

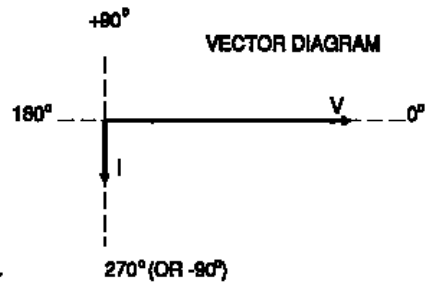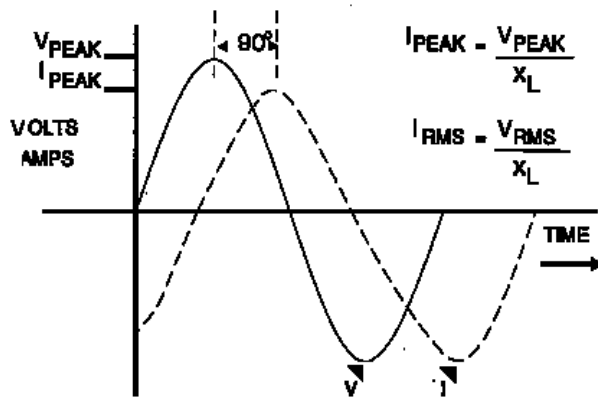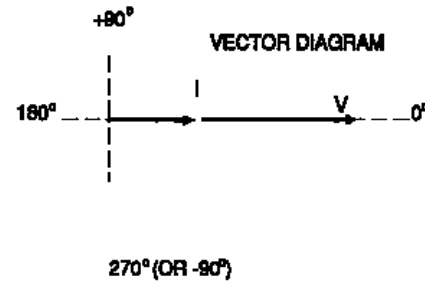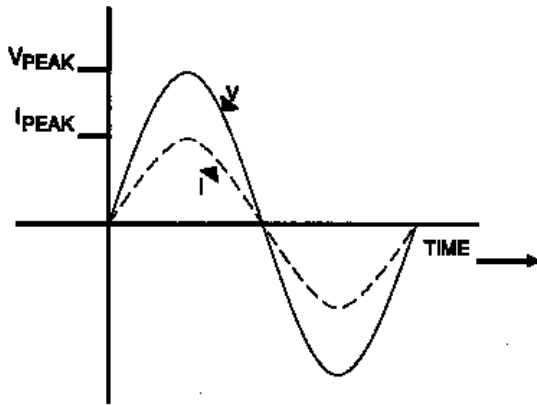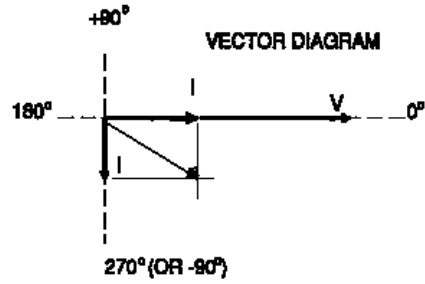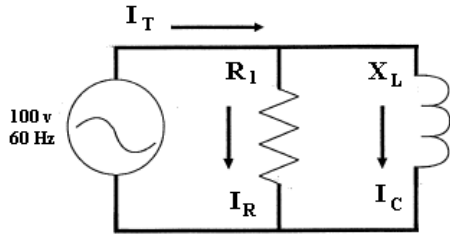(Using the Inductor and Two 52 Watt Light Bulbs)



EXPERIMENT #4

(Using the Inductor and Two 52 Watt Light Bulbs)

1. Determine voltage across the load.
2. Determine current drawn by the load.
3. Calculate VA by Ohms Law.
7. Calculate power by watt load check.
5. Calculate load power factor and phase angle.

Formulas you may want to use.

$$VA = E \cdot I$$

$$P = E \cdot I \cdot \cos$$






$$WATTS = \frac{K_h \cdot Rev. \cdot 3600}{\text{time (sec.)}}$$

$$\frac{\text{Watts}}{VA} = \cos$$

$$\text{COS} \times 100 = \% \text{ Power Factor}$$

EXPERIMENT #5

(Using the Capacitor)

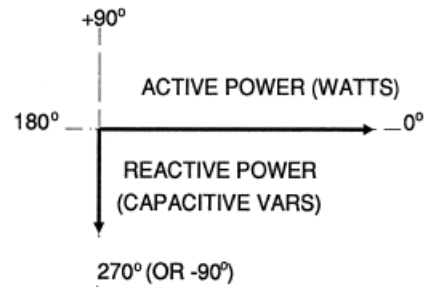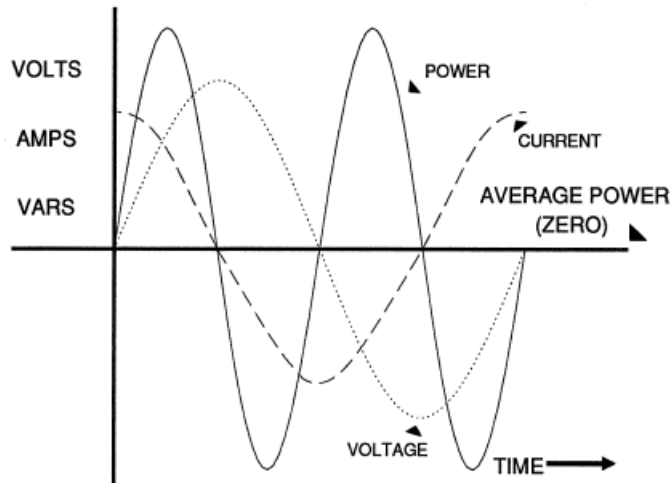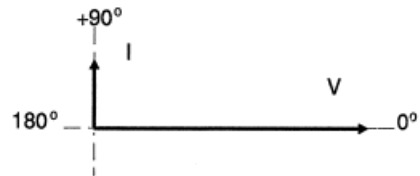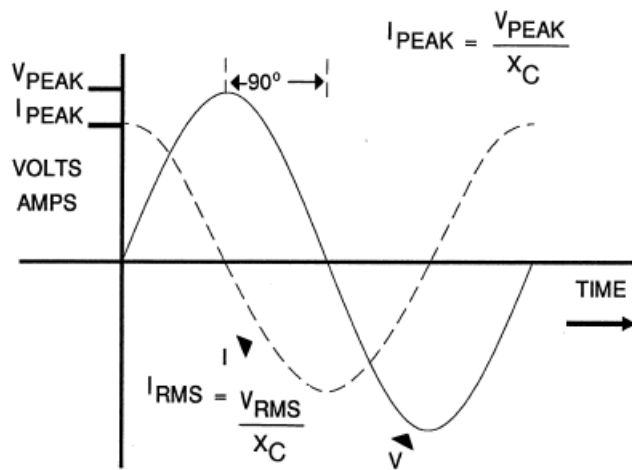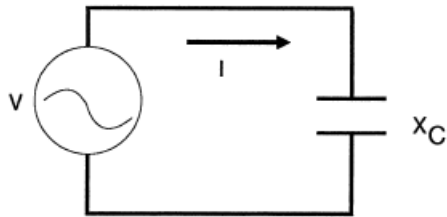

EXPERIMENT #5

(Using the Capacitor)

1. Determine voltage across the load.
2. Determine current drawn by the load.
3. Calculate VA by Ohms Law.
8. Calculate power by watt load check.
5. Calculate load power factor and phase angle.

Formulas you may want to use.

$$VA = E \cdot I$$

$$P = E \cdot I \cdot \cos$$






$$WATTS = \frac{K_h \cdot Rev. \cdot 3600}{\text{time (sec.)}}$$

$$\frac{\text{Watts}}{VA} = \cos$$

$$\text{COS} \times 100 = \% \text{ Power Factor}$$

EXPERIMENT #6

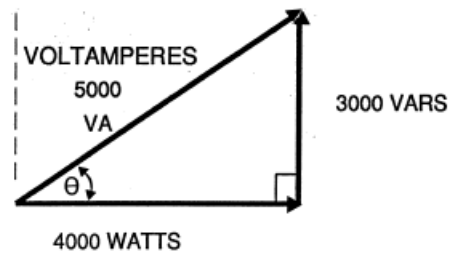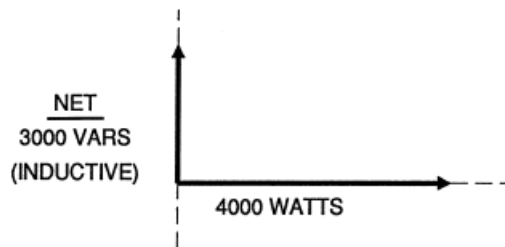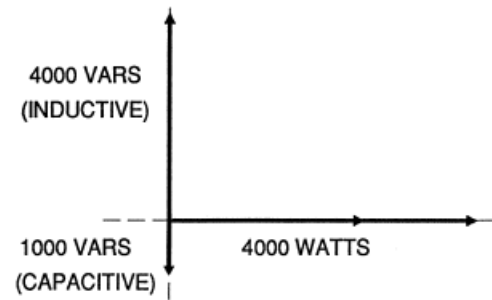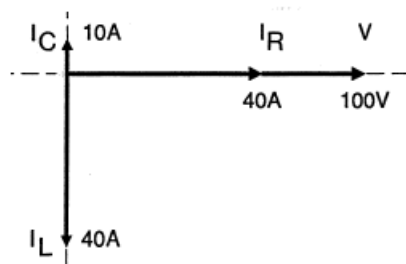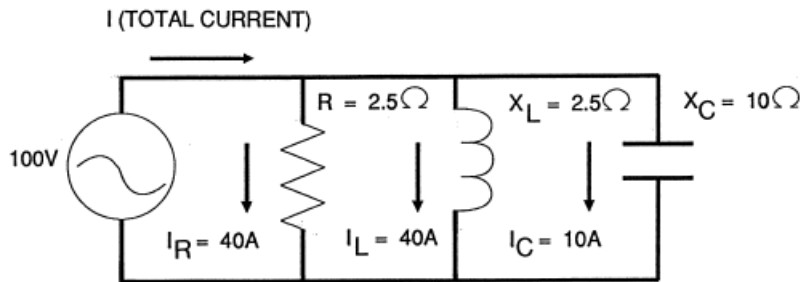(Using the Capacitor, Inductor, and Two 52 Watt Light Bulbs)



$$\text{P.F.} = \frac{\text{WATTS}}{\text{VA}} = \cos \theta$$

EXPERIMENT #6

(Using the Capacitor, Inductor, and Two 52 Watt Light Bulbs)

1. Determine voltage across the load.
2. Determine current drawn by the load.
3. Calculate VA by Ohms Law.
9. Calculate power by watt load check.
5. Calculate load power factor and phase angle.

Formulas you may want to use.

$$VA = E \cdot I$$

$$P = E \cdot I \cdot \cos$$

$$WATTS = \frac{K_h \cdot Rev. \cdot 3600}{\text{time (sec.)}}$$

$$\frac{\text{Watts}}{VA} = \cos$$

$$\text{COS} \times 100 = \% \text{ Power Factor}$$